

**SIPNA COLLEGE OF ENGINEERING AND TECHNOLOGY, AMRAVATI**  
**Department of Computer Science and Engineering**

- Year/Sem: 2<sup>nd</sup>/3<sup>rd</sup>
- Subject: A&DE
- Session: 2022-23

---

**Question Bank**

**Unit-III**

✓ Q1. Convert the given hexadecimal number  $(1E.53)_{16}$  into equivalent binary, octal & decimal.

✓ Q2. Represent  $(32)_{10}$  in  
a) BCD code                      b) Excess-3 Code

✓ Q3. Convert the following binary to Gray code  $(11001100)_2$ .

Q4. Compute using 2's complement  
 $(42)_{10} - (68)_{10}$

✓ Q5. Convert the following octal number into its equivalent hexadecimal, binary & decimal.  
a)  $(0.7634)_8$                       b)  $(65.64)_8$

Q6. Perform following subtraction using 2's Compliments method  
a)  $(2A)_{16} - (1C)_{16}$               b)  $(28)_{10} - (16)_{10}$

✓ Q7. Convert  $(20)_{10}$  to Gray code

✓ Q8. Represent the decimal number 62 in following various codes;  
i) Binary ii) BCD iii) Excess - 3 iv) Gray Code v) Octal vi) Hexadecimal

Q9. Perform following subtraction using 9's Compliments method  
a)  $(28)_{10} - (16)_{10}$               b)  $(34)_{10} - (29)_{10}$

Q10. Perform following subtraction using 10's Compliments method  
a)  $(268)_{10} - (347)_{10}$           b)  $(69)_{10} - (32)_{10}$

✓ Q11. Convert the following numbers:

- i)  $(117)_{10} = ( )_2$
- ii)  $(37.31)_{10} = ( )_2$
- iii)  $(3000.45)_{10} = ( )_8$
- iv)  $(2003.31)_{10} = ( )_{16}$

✓ Q12. Convert the following numbers to its decimal equivalent:

- i)  $(475.25)_8 = ( )_{10}$
- ii)  $(9B2.1A)_{16} = ( )_{10}$
- iii)  $(3102.12)_8 = ( )_{10}$
- iv)  $(614.15)_8 = ( )_{10}$

#### Unit-IV

- Q1. Simplify the following function using k-map  
 $f = \sum m(0,1,2,3,5,7,9) + d(11,13,14,15)$
- Q2. Simplify the following Boolean function by using k-map  
 $F(A, B, C, D) = \sum m(0,1,2,3,5,7,8,9) + d(11, 13, 14, 15)$
- Q3. Simplify the following function using tabulation method  
 $f(A, B, C, D) = \pi M(0,2,4,6,8,9,12,13)$
- Q4. Implement following function with NOR-NOR logic:  
 $f = \pi M(0,2,4,5,6)$
- Q5. Implement following function with NAND-NAND logic:  
 $f = \sum m(0,2,4,5,6)$
- Q6. Simplify the following three variable expression using Boolean function  
 $F = \sum m(1,3,5,7)$
- Q7. Simplify the following Boolean function by using tabulation method  
 $F(A, B, C, D) = \sum m(0,1,2,3,5,7,8,9,11,14)$
- Q8. Simplify the following Boolean function by using tabulation method  
 $F(A, B, C, D, E) = \sum m(0,1,2,3,5,7,8,9,11,14,16,18,20,23,27,28,29,31)$
- Q9. Simplify the following Boolean function by using K-map  
 $F(A, B, C, D, E) = \sum m(0,1,2,3,5,7,8,9,11,14,16,18,20,23,27,28,29,31)$
- Q10. Simplify the following Boolean function by using k-map  
 $F(A, B, C, D) = \pi M(0,1,2,3,5,7,8,9) + d(11, 13, 14, 15)$
- Q11. Prove the following: -
1.  $A + \bar{A}B + \bar{A}\bar{B}C + \bar{A}\bar{B}\bar{C}D + \bar{A}\bar{B}\bar{C}\bar{D}E = A + B + C + D + E$
  2.  $(A + B)(A + C) = A + BC$
  3.  $AB + CD = (A+C)(A+D)(B+C)(B+D)$
- Q12. Solve Using De-Morgans Theorem:
1.  $Z = \overline{(A + BC)(D + EF)}$
  2.  $Z = \overline{A + \bar{B} + \bar{C}D}$
  3.  $Z = \overline{(A + \bar{B}C)} (\bar{A}\bar{B} + ABC)$

**Sipna College of Engineering & Technology, Amravati**  
**Department of Computer Science & Engineering**  
**Question Bank**  
**Unit V & VI**

---

**UNIT-V**

- Q1: Design BCD to Excess-3 code converter using minimum number of logic gates
- Q2: Realise 5-line to 32-line decoder using 4-line to 16-line decoder.
- Q3: Design 7-bit odd parity checker using IC 74180 and explain working.
- Q4: Design a binary to 7-segment decoder using 4:16 line decoder.
- Q5: Design 10-bit even parity generator using single 74180 and inverter.
- Q6: Design a logic circuit to generate an even parity bit for 3-bit binary input.
- Q7: Design 1:32 D-MUX using 1:16 D-MUX
- Q8: Explain decimal to BCD priority encoder.
- Q9: Design a hexadecimal to binary priority encoder using 74148 ICs and one 74157 MUX.
- Q10: Design 32:1 MUX using 16:1 MUX ICs and an OR gate.
- Q11: Design 5-bit comparator using a single 7485 and one gate.
- Q12: Design Binary to Gray code converter
- Q13: Design 4-bit Look Ahead Carry adder and explain its operation.
- Q14: Design Full Adder using K-Map.
- Q15: Design 40:1 multiplexer using 8:1 multiplexers
- Q16: Implement the following function using 4-line to 16-line decoder.  
 $F1 = \sum m(0,1,2,5,7)$ ,  $F2 = \sum m(7,9,10,11,12)$ ,  $F3 = \sum m(8,11,13,14,15)$ .

**UNIT-VI**

- Q1: What is Shift Register? Explain 3-bit shift register along with neat Timing diagram.
  - Q2: Draw a mod - 5 synchronous up - counter using T flip - flop. Explain the same with the help of Timing diagram.
  - Q3: What is race around condition? How does it get eliminated in a master slave J - K flip flop? Explain.
  - Q4: With the help of neat diagram. explain the working of 4bit ring counter, also give the timing diagram.
  - Q5: Draw and explain the operation of 4-bit Bidirectional shift Register
  - Q6: State different types, of shift registers. Explain the operation of 3-bit shift register with neat diagram.
  - Q7: Design a 3-bit synchronous counter using J-K F/F.
  - Q8: Explain the operation of 5- stage twisted ring counter using D F/F.
  - Q9: Design Universal Shift Register and explain its operation.
  - Q10: Draw and explain the circuit diagram for M-S-J-K F/F and explain its advantages over JK F/F.
  - Q11: Explain performance comparison of counters and shift registers.
-

**Sipna College of Engineering & Technology, Amravati**  
**Department of Computer Science & Engineering**  
**Question Bank**  
**Unit I & II**

---

**UNIT-I**

- Q1: Explain the forward and reverse characteristics of p-n junction diode. How it depends on temperature.
- Q2: With respect to a P-N junction explain depletion region.
- Q3: Compare CB, CC, CE with respect to current gain, voltage gain, I/p. resistance, o/p resistance and plot their i/p., o/p characteristics, explain them. Discuss any one application of each configuration
- Q4: State different parameter of BJT. How BJT use as switch in CE mode?
- Q5: Draw and Explain I/p & o/p characteristics of CE configuration amplifier and indicate active, saturation and cut-off region.
- Q6: Derive expression between  $\alpha$  and  $\beta$ . Explain  $I_C = \beta I_B + (1+\beta) I_{CEO}$
- Q7: Explain the operation of PNP and NPN transistor.
- Q8: For a transistor  $\alpha = 0.98$ ;  $I_E = 20\mu A$ ;  $I_{CBO} = 1mA$  find the value of total  $I_C$ ,  $I_B$ ,  $\beta$  and  $I_{CEO}$ .
- Q9: Draw and Explain I/p & o/p characteristics of CB configuration.
- Q10: Explain the operation of transistor in details.
- Q11: Explain the concept of leakage current  $I_{CBO}$  and  $I_{CEO}$ . How are they related with each other
- Q12: For CB configuration if i)  $\alpha = 0.95$  and  $I_E = 1mA$  find the values of  $I_C$  and  $I_B$ , ii)  $I_E = 2mA$  and  $I_B = 20\mu A$  compute the values of  $\alpha$  and  $I_C$ .

**UNIT-II**

- Q1: Static characteristics of JFET explain in detail.
- Q2: With the help of suitable diagram explain Enhancement type MOSFET.
- Q3: With the help of suitable diagram explain depletion type MOSFET.
- Q4: A FET has following parameters,  $I_{DSS} = 32mA$ ;  $V_{GS} (off) = -8V$ ;  $V_{GS} = -4.5V$  find the value of  $I_D$ .
- Q5: Compare MOSFET with JFET.
- Q6: Derive  $\mu = g_m \times r_d$  from the characteristic of JFET.
- Q7: Compare JFET with BJT.
- Q8: Define the various parameters of JFET.
- Q9: A FET has a driven current of  $4mA$ . If  $I_{DSS} = 8mA$  and  $V_{GS} (off) = -6V$ . Find  $V_{GS}$  &  $V_P$ .
- Q10: What is a complementary metal-oxide semiconductor (CMOS)?
-