

## SUMMER-2023

### UNIT-1

**Q.1 a)** With the help of characteristics, explain the operation of PN Junction diode. What is the effect of forward & reverse biasing on depletion region? (7)

**b)** Explain how BJT can be used as amplifier. (7)

**Q.2 a)** Draw & explain input and output characteristics of common emitter configuration of BJT. (7)

**b)** Explain in brief

i) Cut in voltage of diode

ii) Reverse Breakdown voltage.

iii) Peak inverse voltage. (7)

### UNIT-2

**Q.3 a)** Give the comparison of JFET & MOSFET. (7)

**b)** Explain the structure & operation of N-channel depletion type MOSFET. (6)

**Q.4 a)** Explain JFET parameters.

i) Saturation current

ii) Pinch off voltage

iii) Output Admittance (6)

**b)** What are Enhancement & Depletion MOSFETS? Explain construction & operation of Enhancement MOSFET. (7)

### UNIT-3

**Q.5 a)** Convert following numbers to decimal

i)  $(1E2)_{16}$  ii)  $(214)_8$  (7)

**b)** Find subtraction of 110 & 101 using 2's complement method. (6)

**Q.6 a)** Explain decimal number system, Binary number system, octal number system & Hexadecimal number system with example. (6)

iii)  $(1\ 1\ 1\ 1\ 0)_2$  to Excess - 3 code.

**(7)**

## UNIT-4

**Q.7 a)** Solve following logic function using quine McCluskey method.

$$F(x_1, x_2, x_3, x_4) = \Sigma m(0, 1, 3, 8, 9, 11, 15) \quad (13)$$

**Q.8 a)** Reduce following function using k-map & also draw the logic diagram

$$f(x_1, x_2, x_3, x_4) = \sum m(0, 1, 3, 4, 5, 7, 10, 13, 14, 15) \quad (7)$$

**b) Minimize following switching function using k-map**

$$f(A,B,C,D) = \Sigma m(1,3,7,11,15) + d(0,2,5) \quad (6)$$

## UNIT-5

**Q.9 a)** Describe the steps of combinational logic design. Explain with suitable example. **(7)**

**b)** Implement following function using suitable multiplexer

$$f(A,B,C,D) = \Sigma m(0,1,3,4,8,12,14) \quad (7)$$

**Q.10 a)** Explain in detail 4-bit parallel subtractor. **(7)**

**b)** Implement following expression using decoder.

$$\text{i) } f_1 = M(0, 1, 5, 8, 9) \quad \text{ii) } f_2 = M(1, 2, 3, 7, 12, 14) \quad (7)$$

## UNIT-6

**Q.11 a)** Explain synchronous & Asynchronous counter in detail. **(7)**

**b) Convert D flip flop to**

$$\text{i) SR flip-flop} \quad \text{ii) T flip-flop} \quad \text{(6)}$$

**Q.12 a)** Design synchronous MOD-6 counter using JK flip flop. **(6)**

**b)** Convert S-R flip-flop to J-K flip-flop.

**(7)**